

VLSI COE - VLSI Design Methodologies (LAB 1-LAB 6)

LAB 1

HALF ADDER:

RTL CODE:

```
module half_adder(a,
                  b,
                  sum,
                  carry);

    input  a,
           b;
    output sum,
           carry;

    assign sum = a ^ b;
    assign carry = a & b;
endmodule
```

TESTBENCH:

```
module half_adder_tb();
    reg  a,b;
    wire sum,carry;
    integer i;
    //Instantiating the half adder
    half_adder HA1(.a(a), .b(b), .sum(sum), .carry(carry));
    initial
    begin
        a  = 1'b0;
        b  = 1'b0;
    end
    initial
    begin
```

```



for (i=0;i<4;i=i+1)
begin
    {a,b}=i;
    #10;
end
end

initial $monitor("Input a=%b, b=%b, Output sum =%b, carry=%b",
                a,b,sum,carry);

initial #100 $finish;
endmodule

```

OUTPUT:

 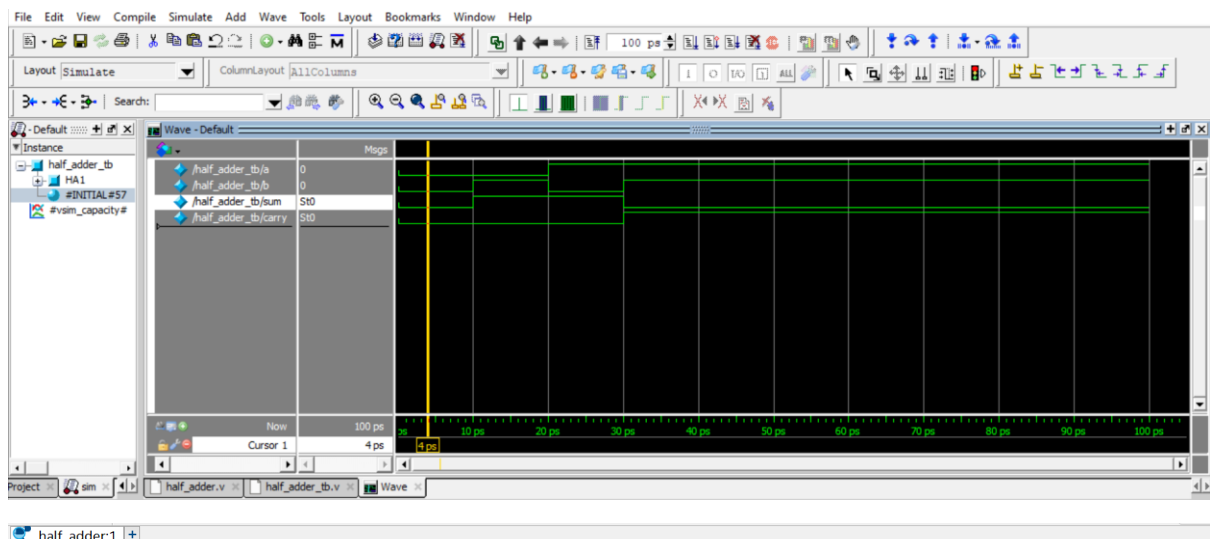

FULL ADDER:**RTL CODE:**

```

module full_adder(a,
                  b,
                  c,
                  sum,
                  carry);

    // Step 1. Write down the directions for the ports
    input a,b,c;
    output sum,carry;

    // Step 2. Declare the internal wires
    wire w1,w2,w3;

    // Step 3. Instantiate two Half-Adders
    half_adder HA1 (.a(a),.b(b),.sum(w1),.carry(w2));
    half_adder HA2 (.a(w1),.b(c),.sum(sum),.carry(w3));

    // Step 4. Instantiate the OR gate
    or or1 (carry,w2,w3);
endmodule

```

TESTBENCH:

```

module full_adder_tb();

    reg  a,b,cin;

    wire  sum,carry;

    integer i;

    //Instantiate the full adder
    full_adder FA1 (.a(a),.b(b),.c(cin),.sum(sum),.carry(carry));

    initial

    begin

        a    = 1'b0;
        b    = 1'b0;
        cin  = 1'b0;

    end

    initial

```

```

begin
    for (i=0;i<8;i=i+1)
    begin
        {a,b,cin}=i;
        #10;
    end
end



initial $monitor("Input a=%b, b=%b, c=%b, Output sum =%b,
carry=%b",a,b,cin,sum,carry);


initial #100 $finish;

endmodule

```

OUTPUT:

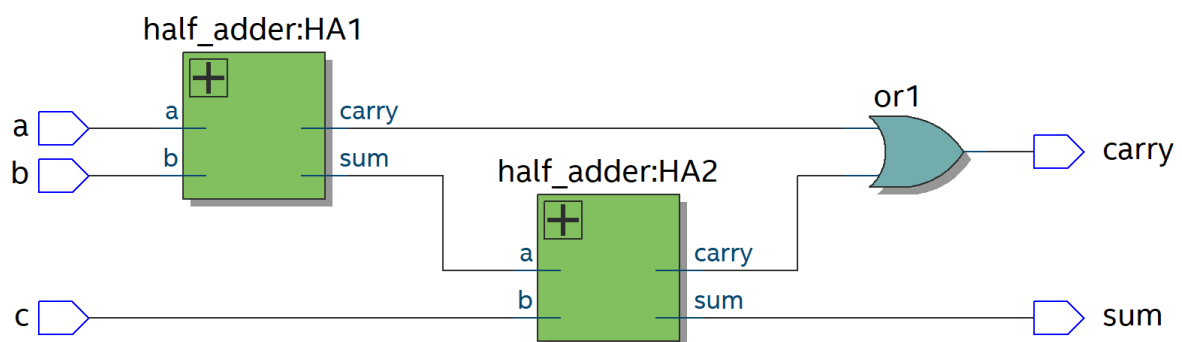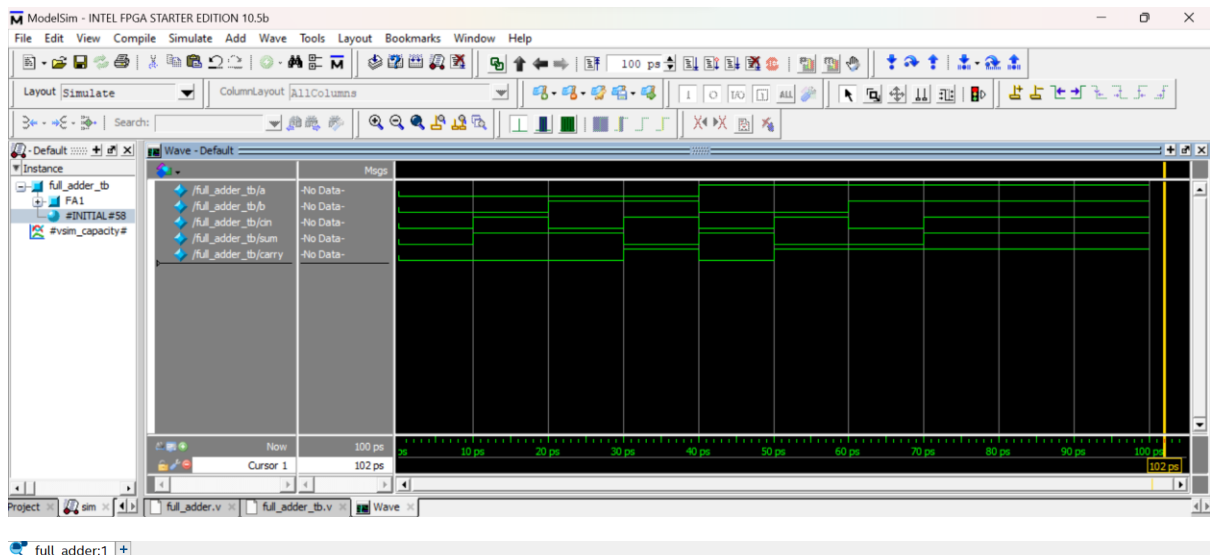

 **LAB 2:**

Arithmetic logic unit executing 16 operations:

RTL CODE:

```

module alu(a,
           b,
           command,
           oe,
           y);

    parameter ADD = 4'b0000, // Add two 4 bit numbers a and b.
           INC = 4'b0001, // Increment a by 1.
           SUB = 4'b0010, // Subtracts b from a.
           DEC = 4'b0011, // Decrement a by 1.
           MUL = 4'b0100, // Multiply 4 bit numbers a and b.
           DIV = 4'b0101, // Divide a by b.
           SHL = 4'b0110, // Shift a to left side by 1 bit.
           SHR = 4'b0111, // Shift a to right by 1 bit.
           AND = 4'b1000, // Logical AND
           OR = 4'b1001, // Logical OR
           INV = 4'b1010, // Complement
           NAND = 4'b1011, // Logical NAND

```

```

        NOR  = 4'b1100, // Logical NOR
        XOR  = 4'b1101, // Logical EXOR
        XNOR = 4'b1110, // Logical EXNOR
        BUF  = 4'b1111; // Buffer

input [7:0] a,
        b;

input [3:0] command;

input oe;

output [15:0] y;

reg      [15:0] out;

// Step 1. Write down the functionality of ALU based on commands
given above.

//          *Use arithmetic and logical operators

always@(*)
begin
    case (command)
        //----- write the functionality here -----
        ADD   :    out  =a+b;
        INC   :    out  =a+1;
        SUB   :    out  =a-b;
        DEC   :    out  =a-1;
        MUL   :    out  =a*b;
        DIV   :    out  =a/b;
        SHL   :    out  =a<<b;
        SHR   :    out  =a>>b;
        AND   :    out  =a&b;
        OR    :    out  =a|b;
        INV   :    out  =~a;
        NAND  :    out  =~(a&b);
        NOR   :    out  =~(a|b);
        XOR   :    out  =a^b;
        XNOR  :    out  =~(a^b);
        BUF   :    out  =a;
    endcase
end

```

```

        default :      out      =16'hxxxx;

    endcase

end

// Step 2. Understand the tri-state output logic

    assign y = (oe) ? out : 16'hzzzz;

endmodule

```

TESTBENCH:

```

module alu_tb();

    reg [7:0]  a,

                b;

    reg [3:0]  command;

    reg enable;

    wire [15:0] y;

    integer m,n,o;

    parameter ADD  = 4'b0000, // 0  Add two 4 bit numbers a and b.
                INC  = 4'b0001, // 1  Increment a by 1.
                SUB  = 4'b0010, // 2  Subtracts b from a.
                DEC  = 4'b0011, // 3  Decrement a by 1.
                MUL  = 4'b0100, // 4  Multiply 4 bit numbers a and b.
                DIV  = 4'b0101, // 5  Divide a by b.
                SHR  = 4'b0110, // 6  Shift a to left side by 1 bit.
                SHL  = 4'b0111, // 7  Shift a to right by 1 bit.
                AND  = 4'b1000, // 8  Logical AND
                OR   = 4'b1001, // 9  Logical OR
                INV  = 4'b1010, // 10 Compement
                NAND = 4'b1011, // 11 Logical NAND
                NOR  = 4'b1100, // 12 Logical NOR
                XOR  = 4'b1101, // 13 Logical EXOR
                XNOR = 4'b1110, // 14 Logical EXNOR
                BUF  = 4'b1111; // 15 Buffer

    reg [(4*8)-1:0] string_cmd;

// Step 1. Instantiate the design ALU

    alu DUT(a,b,command,enable,y);

```

```
// Step 2. Write a task named "initialize" to initialize the inputs  
of DUT
```

```
task initialize;  
begin  
    {a,b,command,enable}=0;  
end  
endtask
```

```
// Step 3. Understand the complete test bench and various tasks  
defined below.
```

```
task en_oe(input i);  
begin  
    enable=i;  
end  
endtask  
task inputs(input [7:0] j,k);  
begin  
    a=j;  
    b=k;  
end  
endtask  
task cmd (input [3:0] l);  
begin  
    command=l;  
end  
endtask  
task delay();  
begin  
    #10;  
end  
endtask  
always@(command)  
begin  
    case (command)
```



```
        ADD    : string_cmd = "ADD";
        INC    : string_cmd = "INC";
        SUB    : string_cmd = "SUB";
        DEC    : string_cmd = "DEC";
        MUL    : string_cmd = "MUL";
        DIV    : string_cmd = "DIV";
        SHR    : string_cmd = "SHR";
        SHL    : string_cmd = "SHL";
        AND    : string_cmd = "AND";
        OR     : string_cmd = "OR";
        INV    : string_cmd = "INV";
        NAND   : string_cmd = "NAND";
        NOR    : string_cmd = "NOR";
        XOR    : string_cmd = "XOR";
        XNOR   : string_cmd = "XNOR";
        BUF    : string_cmd = "BUF";
    endcase
end
initial
begin
    initialize;
    en_oe(1'b1);
    for (m=0;m<16;m=m+1)
    begin
        for (n=0;n<16;n=n+1)
        begin
            inputs(m,n);
            for (o=0;o<16;o=o+1)
            begin
                command=o;
                delay;
            end
        end
    end
end
```

```

        end

    end

    en_oe(0);

    inputs(8'd20,8'd10);

    cmd(ADD);

    delay;

    en_oe(1);

    inputs(8'd25,8'd17);

    cmd(ADD);

    delay;

    $finish;



end

    initial $monitor("Input oe=%b, a=%b, b=%b, command=%s, Output
y=%b",enable,a,b,string_cmd,y);

endmodule

```

OUTPUT:

 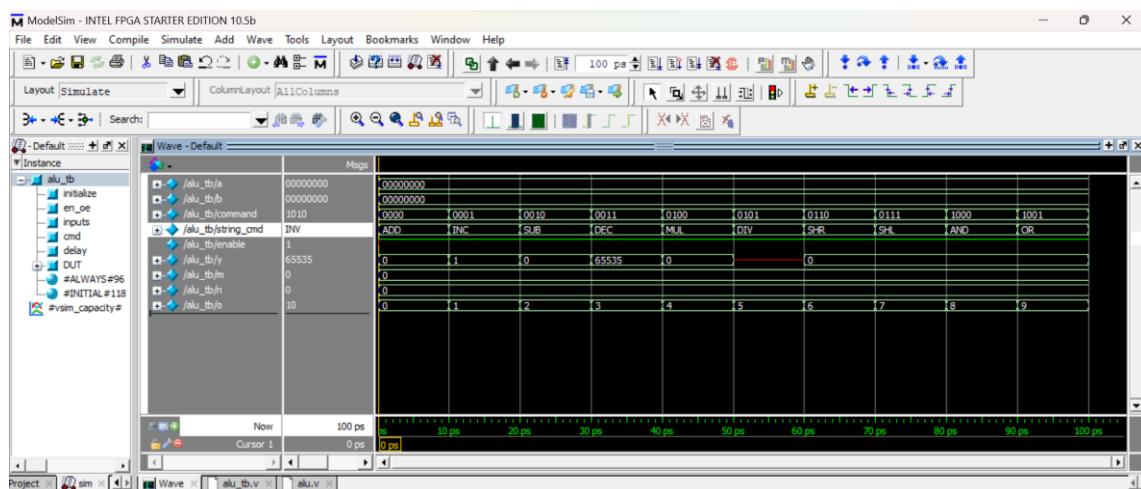

LAB 3:**4:1 MUX Design****RTL CODE:**

```
module mux4_1(a,
              sel,
              y);

// Step 1 : Define the port directions with proper datatypes and
// ranges.

    input [3:0] a;
    input [1:0] sel;
    output reg y;

// Step 2 : Write the MUX behaviour as a parallel logic using case
// statement in behaviour modelling.

    always@(*)
    begin
        case(sel)
            2'd0:y=a[0];
            2'd1:y=a[1];
            2'd2:y=a[2];
            2'd3:y=a[3];
        endcase
    end
endmodule
```

TESTBENCH:

```
module mux4_1_tb();

// Declaration of the variables required for testbench

    reg [1:0] sel;
    reg [3:0] a;
    wire y ;

// Declaration of internal variables required for testbench

    integer i,j;

// Step 1. Instantiate the Design
```

```
    mux4_1 DUT(.a(a),.sel(sel),.y(y));

// Step 2. Define the body for the initialize task to initialize the
variables of DUT to 0

    task initialize;
begin
    a=0;
    sel=0;
end
endtask

// Step 3. Declare tasks with arguments for driving stimulus to DUT

    task select(input [1:0]s);
begin
    sel=s;
end
endtask

    task inps(input [3:0] data);
begin
    a=data;
end
endtask

// Step 4. Call the tasks from procedural block

    initial
begin
    initialize;
    #10;
    for(i=0;i<4;i=i+1)
begin
    select(i);
    for(j=0;j<16;j=j+1)
begin
    inps(j);
    #10;
end
end
end
```

```

end

end

// Step 5. Use $monitor task in a parallel initial block to display
inputs and outputs

initial

    $monitor("a[3:0]=%b--select=%b--y=%d\n",a,sel,y);

// Step 6. Use $finish task to finish the simulation in a parallel
initial

// block with appropriate delay



initial

    #800 $finish;

endmodule

```

OUTPUT:

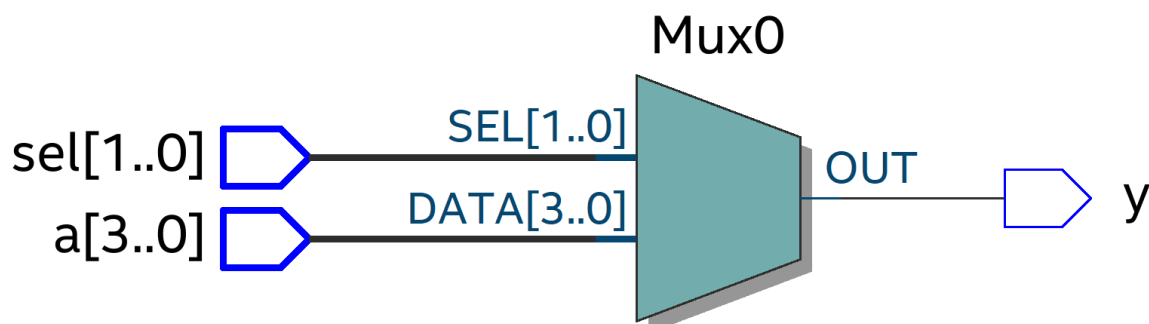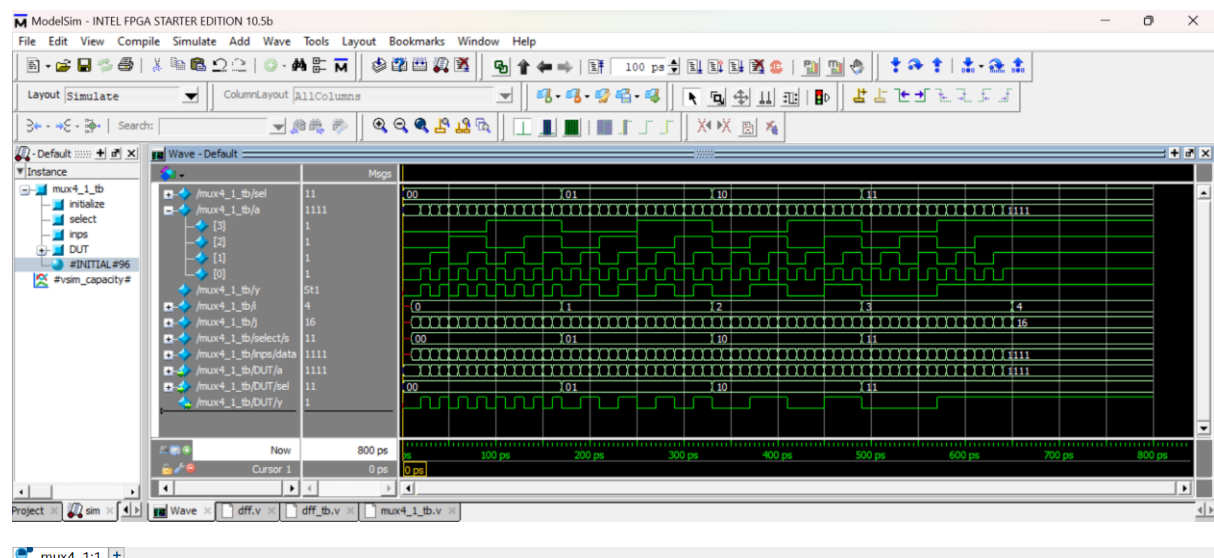

LAB 4:**Delay Flipflop****RTL CODE:**

```
module d_ff(clk,
            reset,
            d,
            q,
            qb);

// Step1 : Declare Port Directions
    input clk,reset,d;
    output reg q;
    output qb;

// Step2 : Write the behavioral logic for D flip-flop functionality.
    always@(posedge clk)
    begin
        if(reset)
            q=0;
        else
            q=d;
    end

//Step3. Assign complement of q to qb.
    assign qb=~q;
endmodule
```

TESTBENCH:

```
module dff_tb();

// Step 1. Define a parameter with name "cycle" which is equal to 10
    parameter cycle=10;

    reg clk,
        reset,
        d;

    wire q,
        qb;
```

```
// Step 2. Instantiate the dff design
d_ff DUT (.clk(clk),.reset(reset),.d(d),.q(q),.qb(qb));
// Step 3. Understand the clock generation logic
always
begin
    #(cycle/2);
    clk = 1'b0;
    #(cycle/2);
    clk=~clk;
end
//Step4. Understand the various tasks used and also how to use tasks
in testbench.

task rst_dut();
begin
    reset=1'b1;
    #10;
    reset=1'b0;
end
endtask

task din(input i);
begin
    @(negedge clk);
    d=i;
end
endtask

initial
begin
    rst_dut;
    din(0);
    din(1);
    din(0);
    din(1);
    din(1);
end
```

```

rst_dut;

din(0);

din(1);

#10;

$finish;

end

// Step 5. Use $monitor task in a parallel initial block to display
inputs and outputs



initial

    $monitor("d=%d--q=%d--qb=%d",d,q,qb);

endmodule

```

OUTPUT:

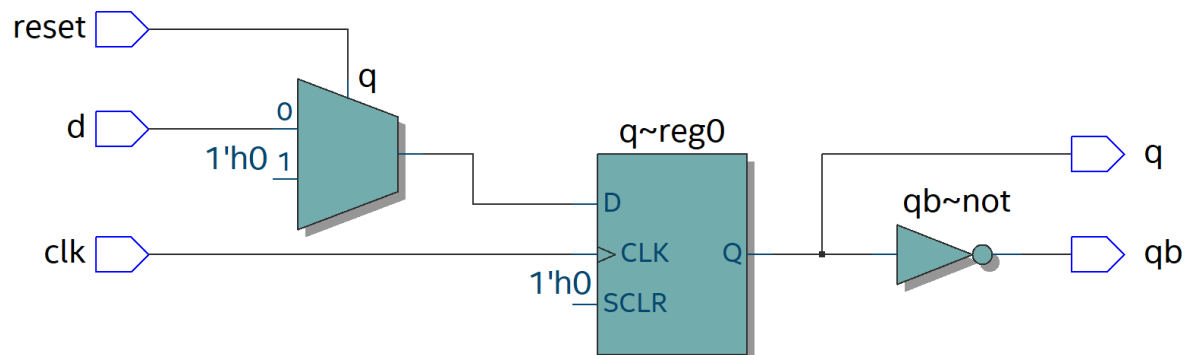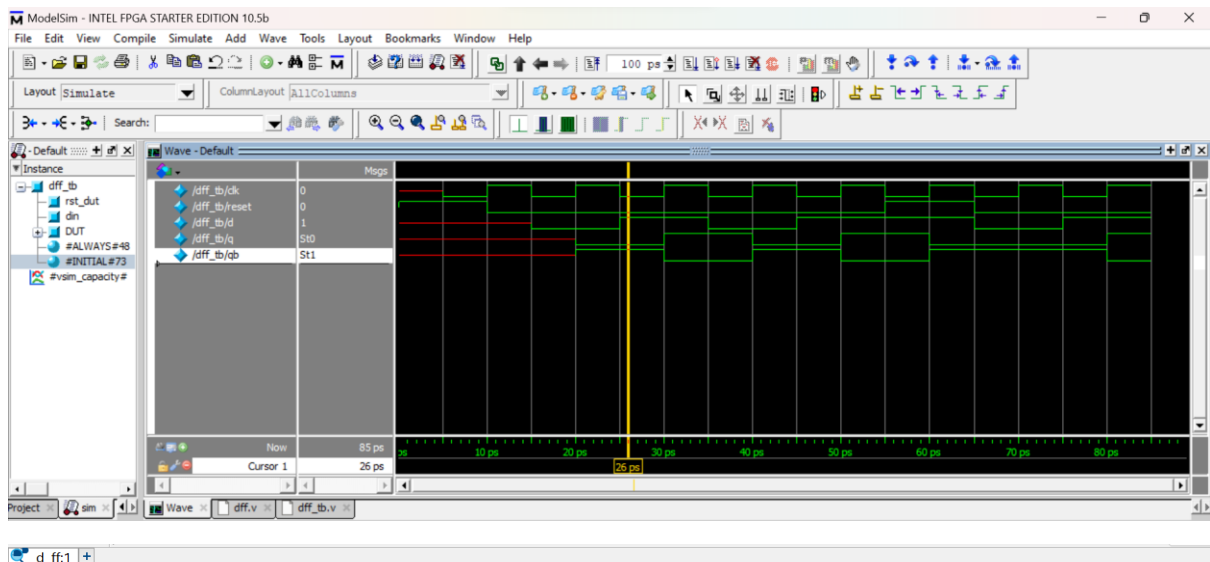

LAB 5:**Asynchronous Single port Random access memory (16x8)****RTL CODE:**

```

module ram(data,
           we,
           enable,
           addr);

    input we,enable;
    input [3:0] addr;
    inout [7:0] data;

    // Step 1. Declare a 8 bit wide memory having 16 locations.
    reg [7:0]mem[15:0];

    // Step 2. Understand the logic for writing data into a memory
    location

    always@(data,we,enable,addr)
        if (we && !enable)
            mem[addr]=data;

    // Step 3. Understand the logic of reading data from a memory
    location

    assign data= (enable && !we) ? mem[addr] : 8'hzz;
endmodule

```

TESTBENCH:

```

module ram_tb;

    wire [7:0] data;
    reg [3:0] addr;
    reg we,enable;
    reg [7:0] tempd;
    integer l;

    // Step 1. Instantiate the RAM module and connect the ports
    ram DUT(data,we,enable,addr);

    assign data=(we && !enable) ? tempd : 8'hzz;

    task initialize();

```

```

begin
    we=1'b0; enable=1'b0; tempd=8'h00;
end
endtask

// Step 2. define body of the task named "stimulus" to initialize
the
//          "addr" and "tempd" inputs through i and j variables.
//          use i initialization for "addr" and j initialization
for "tempd".
task stimulus(input [3:0]i,input [7:0]j);
begin
//----- define the body of the task here-----//
    addr=i;
    tempd=j;
end
endtask

// Step 3. Understand the various tasks defined in this testbench
task write();
begin
    we=1'b1;
    enable=1'b0;
end
endtask

task read();
begin
    we=1'b0;
    enable=1'b1;
end
endtask

task delay;
begin
    #10;
end

```

```

endtask

initial
begin
    initialize;

    delay;

    write;

    for(l=0;l<16;l=l+1)
    begin
        stimulus(l,l);

        delay;
    end

    initialize;

    delay;

    read;

    for(l=0;l<16;l=l+1)
    begin
        stimulus(l,l);

        delay;
    end

    end

    delay;


    $finish;


end

endmodule

```

OUTPUT:

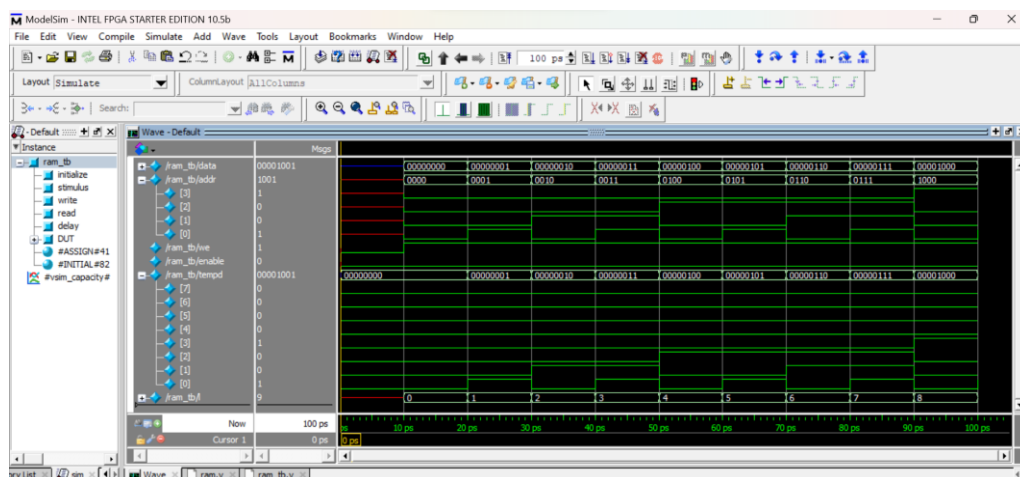

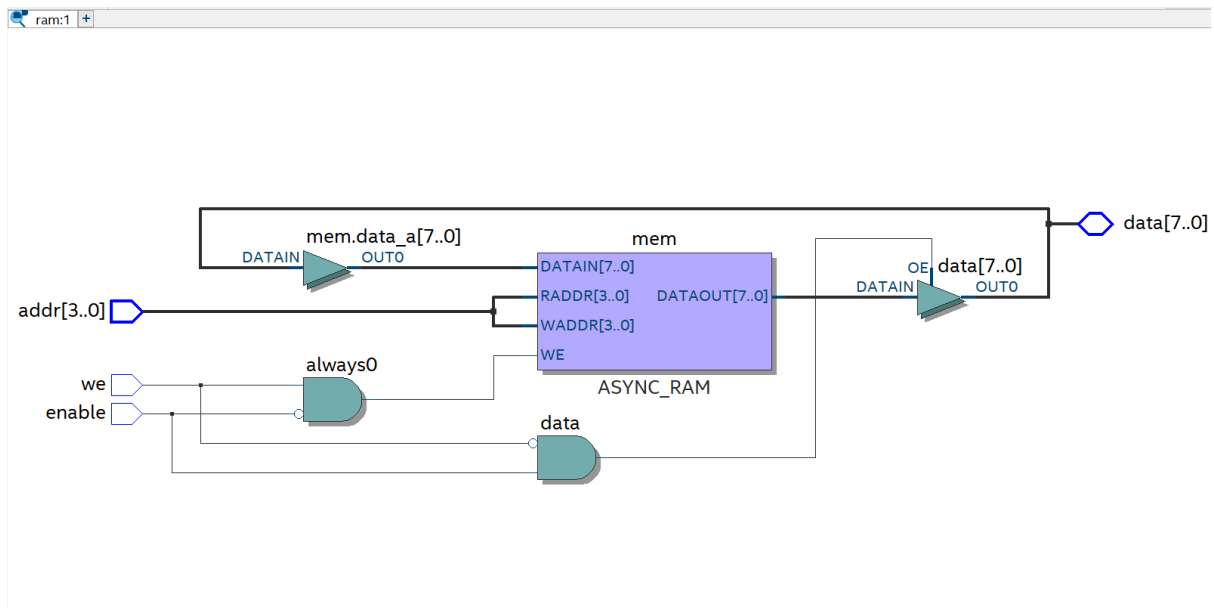

LAB 6:

Sequence detector detecting "101"

RTL CODE:

```

module seq_det(din,
               clock,
               reset,
               dout);

// Step 1. Declare the states as parameter
"IDLE", "STATE1", "STATE2", "STATE3",

//           and use binary encoding for encoding these states.
parameter IDLE = 2'b00,
           STATE1 = 2'b01,
           STATE2 = 2'b10,
           STATE3 = 2'b11;

// Step 2. Write down the port direction with proper directions.
input din, clock, reset;
output dout;
reg [1:0] present_state, next_state;

// Step 3. Write down the sequential logic for present state
always@(posedge clock)
begin

```

```

    if(reset)
        present_state <= IDLE;
    else
        present_state <= next_state;
    end
// Step 4. Understand the combinational logic for next state
always@(present_state,din)
begin
    case (present_state)
        IDLE    : if (din==1)
                    next_state=STATE1;
                else
                    next_state=IDLE;
        STATE1 : if (din==0)
                    next_state=STATE2;
                else
                    next_state=STATE1;
        STATE2 : if (din==1)
                    next_state=STATE3;
                else
                    next_state=IDLE;
        STATE3 : if (din==1)
                    next_state=STATE1;
                else
                    next_state=STATE2;
        default : next_state=IDLE;
    endcase
end
// Step 5. Write down the logic for output "dout".
    assign dout = (present_state == STATE3);
endmodule

```

TESTBENCH:

```
module seq_det_tb();  
    parameter cycle=10;  
    reg  din,  
        clock,  
        reset;  
    wire dout;  
    seq_det SQD(.din(din),  
                .clock(clock),  
                .reset(reset),  
                .dout(dout));  
  
    // Step 1. Generate clock, using parameter "cycle"  
    initial  
    begin  
        clock=0;  
        forever #(cycle/2) clock=~clock;  
    end  
  
    // Step 2. Write a task named "initialize" to initialize  
    //          the input din of sequence detector.  
    task initialize;  
    begin  
        din = 0;  
    end  
    endtask  
  
    task delay(input integer i);  
    begin  
        #i;  
    end  
    endtask  
  
    // Step 3. Write a task named "RESET" to reset the design,  
    //          use the above delay task for adding delay  
    task RESET;
```

```

begin
    reset=1;
    delay(10);
    reset=0;
end

endtask

// Step 4. Write a task named "stimulus" which provides input to
//          design on negedge of clock
task stimulus(input j);
begin
    @(negedge clock)
    din = j;
end
endtask

// Step 5 : understand the remaing logic defind below.
initial $monitor("Reset=%b, state=%b, Din=%b, Output Dout=%b",
                reset,SQD.present_state,din,dout);
always@(SQD.present_state or dout)
begin
    if (SQD.present_state==2'b11 && dout==1)
        $display("Correct output at state %b", SQD.present_state);
end

initial
begin
    initialize;
    RESET;
    stimulus(0);
    stimulus(1);
    stimulus(0);
    stimulus(1);
    stimulus(0);
    stimulus(1);
end

```

```

stimulus(1);

RESET;

stimulus(1);

stimulus(0);

stimulus(1);

stimulus(1);

delay(10);

$finish;

end

endmodule

```

OUTPUT:

